

BRAC UNIVERSITY
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING
COURSE NO.: CSE250
Circuits and Electronics Laboratory

EXPT. NO. 3

Name Of The Experiment:

Verification of Superposition Principle

OBJECTIVE:

To verify experimentally the Superposition theorem which is an analytical technique of determining currents in a circuit with more than one emf source.

THEOREM:

In a linear circuit containing multiple independent sources and linear elements (e.g. resistors, inductors, capacitors) the voltage across (or the current through) any element when all the sources are acting simultaneously may be obtained by adding algebraically all the individual voltages (or the currents) caused by each independent source acting alone, with all other sources deactivated.


An independent voltage source is deactivated (made zero) by shorting it and an independent current source is deactivated (made zero) by open circuiting it. However, if a dependent source is present it must remain active during the superposition process.

APPARATUS :


- Two DC power supplies.
- One multimeter.

PROCEDURES :


- 1) Set up the circuit as in Fig. 1.

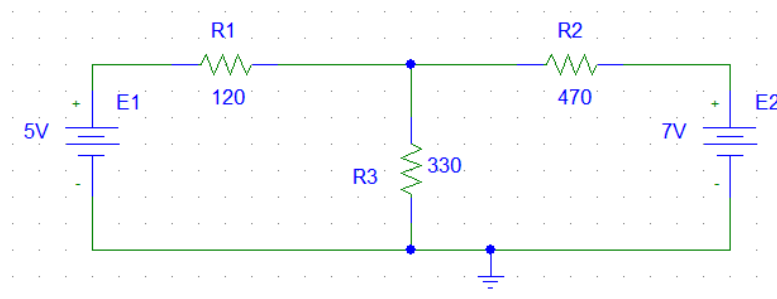

When E₂ active:

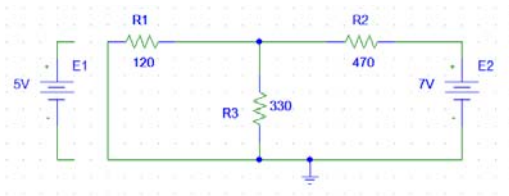

When E₁ active:

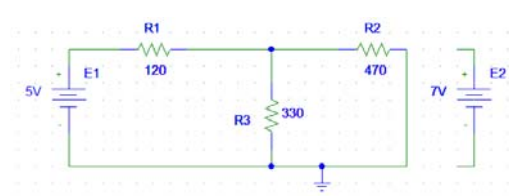

- 2) Apply 5 volts from E₁ and 7 volts from E₂.
- 3) Measure the current I and record it in the given table.
- 4) Render E₂ inactive (keeping E₁ active) & measure the current I' in the branch R₃.
- 5) Render E₁ inactive (keeping E₂ active) & Measure the current I'' in the branch R₃.
- 6) Verify if $I = I' + I''$ which would validate the superposition theorem for this particular circuit.

TABLE:

No. of Obs.	R ₁ (ohms)	R ₂ (ohms)	R ₃ (ohms)	I ₂ with both E ₁ and E ₂ active (amps)	I ₂ ' with only E ₁ active (amps)	I ₂ '' with only E ₂ active (amps)	I ₂ ' + I ₂ ''
1.	100Ω	220Ω	470Ω				
2.	1.2KΩ	2.2KΩ	3.3KΩ				

REPORT :

1. Show results in tabular form.
2. Comment on the obtained results and discrepancies (if any).

CAUTIONS:

1. Don't switch on the supply until the circuit has been checked by your teacher.
2. Take care of the reading of the apparatus.
3. Take care of any bare circuit element in energized condition.

QUESTION:

1. Define linear element, nonlinear element, linear circuit & nonlinear circuit.
2. "Although Superposition Principle can be used to determine voltage and current in a linear circuit, it cannot be used to determine power." --- Elucidate the statement.
3. Why an independent voltage source is deactivated by short circuiting it and an independent current source is deactivated by open circuiting it?
4. Find analytically the current I using
 - Superposition Principle
 - Mesh Current Method
 - Node Voltage Method

for E₁ = 5 volts, E₂ = 7 volts and R₁, R₂, R₃ at their values recorded in the observation of the Table shown.