

Name: Ms Rodry Tahmid

ID: 20101021

Course Code: Cse250

Experiment No: 3

Experiment Name:

Verification of KCL & KVL

Ans: 3.1

① Objective:

This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of Series Circuits.

② Apparatus:

↳ ~~DC power supplies~~

↳ ~~Resistors~~

↳ ~~Ground / Earthing~~

↳ One DC Ammeter (0-1A)


↳ One multimeter

↳ Three Resistors

↳ One DC power supply

③ Circuit / Block / System Diagram:

Figure-1: KVL verification.

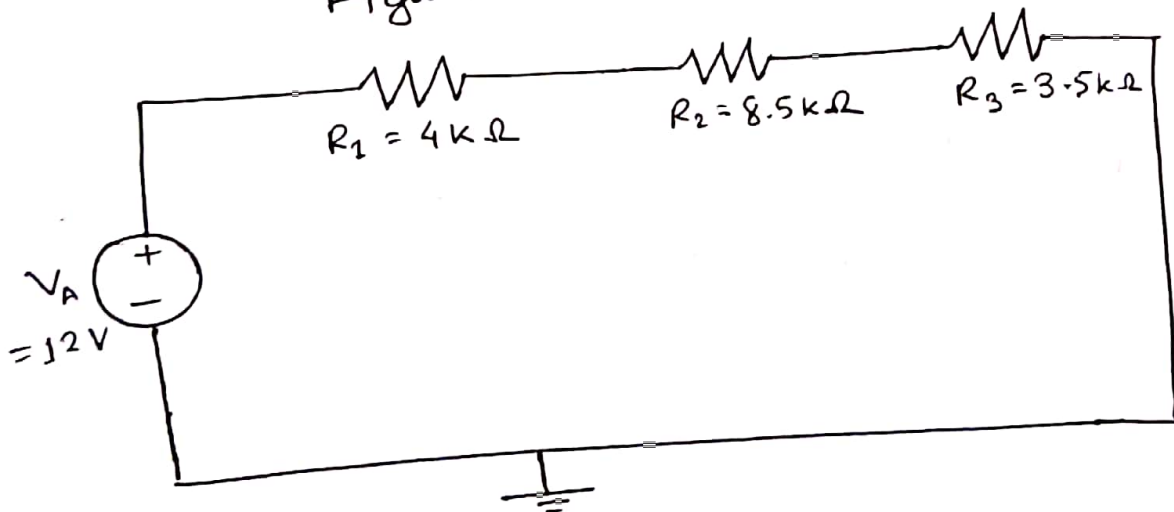

$$V_1 = 12 - 9 = 3V$$

$$V_2 = 9 - 2.625 = 6.375V$$

$$V_3 = 2.625 - 0 = 2.625V$$

$$V_1 + V_2 + V_3 = 3 + 6.375 + 2.625V$$
$$= 12V$$

3.1

④ Result / Analysis:

$$(i) \quad V_1 = 12 - 9 = 3$$

$$V_2 = 9 - 2.625 = 6.375$$

$$V_3 = 2.625 - 0 = 2.625$$

(ii) Done in PSpice.

(iii) KVL Verification:

Observation	R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	V_A (V)	V_1 (V)	V_2 (V)	V_3 (V)
Simulation	4	8.5	3.5	12	3	6.375	2.625
Theoretical	4	8.5	3.5	12	3	6.375	2.625

$V_1 + V_2 + V_3$ (V)
12
12

(i) Theoretical:

$$R = 4 + 8.5 + 3.5 = 16 \text{ k}\Omega = 16 \times 10^3 \Omega$$

$$I = \frac{V}{R} = \frac{12}{16 \times 10^3} = 7.5 \times 10^{-4} \text{ A}$$

$$V_1 = IR_1 = (7.5 \times 10^{-4}) (4 \times 10^3) = 3$$

$$V_2 = IR_2 = (7.5 \times 10^{-4}) (8.5 \times 10^3) = 6.375$$

$$V_3 = IR_3 = (7.5 \times 10^{-4}) (3.5 \times 10^3) = 2.625$$

$$V_1 + V_2 + V_3 = 3 + 6.375 + 2.625 = 12$$

⑤ Questions & Answers:

Q1) What does KVL predict about the circuit?

Ans: $V_A = V_1 + V_2 + V_3$

Q2) Does your calculation of $V_1 + V_2 + V_3$ match the value of V_A ?

Ans: Matches exactly.

⑥ Discussion:

All the results are exactly ^{the} same both in simulation and theory which does not usually happen in practical (Applied Physics).

Ground / Earthing is done in simulation in Pspice for both the figures as it is necessary. (otherwise Pspice wouldn't work).

Ans: 3.2

① Objective:

This experiment is intended to verify Kirchhoff's current law (KCL) with the help of a simple parallel circuit.

② Apparatus:

- ↳ One DC Ammeter (0-1A)
- ↳ Three Resistors
- ↳ One multimeter
- ↳ One DC power

③ no. done later.

④ Result / Analysis:

(i) $V = IR \Rightarrow I = \frac{V}{R}$

$$I = \frac{V_A}{R}$$

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


$$\frac{1}{R_p} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_p = \frac{R_1 + R_2 + R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$$

$$= \frac{4 + 8.5 + 5.5}{(8.5 \times 5.5) + (4 \times 5.5) + (4 \times 8.5)}$$

③ → Continuation ^{3.2} Circuit / Block / System Diagram: ⑥

Figure - 2: KCL Verification.

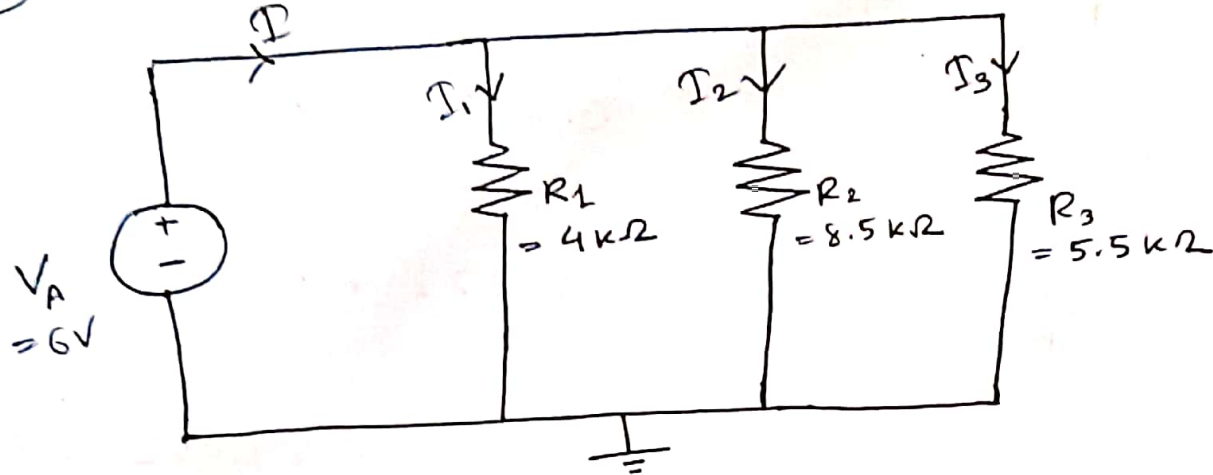

$$I = 3.297 \text{ mA}$$

$$I_2 = 1.500 \text{ mA}$$

$$I_3 = 0.70588 \text{ mA}$$

$$I_1 + I_2 + I_3 = 1.5 + 0.70588 + 1.091 = 3.29688$$

④ → Continuation.

$$R_p = 0.17518$$

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{8.5} + \frac{1}{5.5}$$

$$\frac{1}{R_p} = \frac{411}{748} \Rightarrow R_p = \frac{748}{411} = 1.8199 \approx 1.82 \text{ k}\Omega$$

$$\therefore I = \frac{V_A}{R_p} = \frac{6 \text{ V}}{1.82 \text{ k}\Omega} = 3.2967 \text{ mA}$$

4i) → cont.

(7)

$$I_1 = \frac{V}{R_1} = \frac{3.2}{4} = 1.5 \text{ mA}$$

$$I_2 = \frac{V}{R_2} = \frac{6}{8.5} = 0.70588 \text{ mA}$$

$$I_3 = \frac{V}{R_3} = \frac{6}{5.5} = 1.091 \text{ mA}$$

$$I_1 + I_2 + I_3 = 1.5 + 0.70588 + 1.091 \text{ mA} \\ = 3.29688 \text{ mA}$$

(ii) Done in PSpice.

(iii) KCL verification:

Observation	R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	$\sum I$ (mA)	I_1 (mA)	I_2 (mA)	I_3 (mA)
Simulation	4	8.5	5.5	3.297	1.5	0.70588	1.091
Theoretical	4	8.5	5.5	3.2967	1.5	0.70588	1.091

$I_1 + I_2 + I_3$ (mA)
3.29688
3.29688

(5) Questions & Answers :

Q1) What does KCL predict about the circuit?

Ans: $I = I_1 + I_2 + I_3$.

Q2) Does your calculation of $I_1 + I_2 + I_3$ matches the value of I ?

Ans: Close enough.

(6) Discussion:

Due to change in decimal places, i.e. three decimal places taken in simulation and whereas four decimal places taken in theoretical value, precision is not obtained, i.e., the results are close enough but ~~not exactly~~ does not match exactly.